

ELE 202

Electric Circuit Analysis


LAB COVER PAGE for Part I submission.

Lab #:	2	Lab Title:	Basic concepts, Relationships and Laws of Electrical Circuits.
--------	---	------------	--

Last Name:	Malik
------------	-------

First Name:	Hamza
-------------	-------

Student #:	501112545
------------	-----------

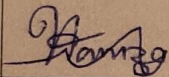Signature:	
------------	---

Section #:	22
Submission date and time:	Feb 3, 2022, 12:55am
Due date and time:	Feb 3, 2022, 2pm

Document submission for Part I:

- A completed and signed "COVER PAGE – Part I" has to be included with your submission. The report will not be graded if the signed cover page is not included.
- Your completed handwritten pages of **Section 4.0** should be scanned (via a scanner or phone images), together with the required MultiSIM images. **Note:** MultiSIM results must be generated using the Department's licensed version of MultiSIM, and the captured screenshots should show your name (at the center-top) and the timestamp (at the bottom-right corner of your screen).
- Collate and create a **.pdf** or **.docx** file of the above, and upload it via D2L **any time prior to the start of your scheduled lab**. Upload instructions are provided on D2L.

Zero marks will be assigned for the entire lab if this Part I is not submitted prior to your scheduled lab.

**By signing above, you attest that you have contributed to this submission and confirm that all work you have contributed to this submission is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: www.ryerson.ca/senate/current/pol60.pdf.*

3.0 REQUIRED LAB EQUIPMENT & PARTS

- Digital Multimeter (DMM) and Power Supply
- ELE202 Lab Kit:- various components, breadboard, wires and jumpers.

4.0 PRE-LAB: ASSIGNMENT

(a) I - V Characteristics of Ohmic Resistor using a simple D.C. Circuit

- (i) Assume varying values of the DC source-voltage, E applied as shown in **Figure 2.0a**. For each source-voltage value, use Ohm's Law to determine the corresponding value of the current, I_R when the resistance, R is $2.2\text{ k}\Omega$ and when it is $3.3\text{ k}\Omega$. Record your theoretical results in **Table 2.0**. Use the space below to show your work.

Pre-Lab workspace

$$\begin{aligned} \textcircled{1} I &= \frac{V}{R} = \frac{3V}{2.2\text{ k}\Omega} = 0.0013636\text{ A} = 1.364\text{ mA} \\ \textcircled{2} I &= \frac{V}{R} = \frac{6V}{2.2\text{ k}\Omega} = 0.002727\text{ A} = 2.727\text{ mA} \\ \textcircled{3} I &= \frac{V}{R} = \frac{9V}{2.2\text{ k}\Omega} = 0.0040909\text{ A} = 4.091\text{ mA} \\ \textcircled{4} I &= \frac{V}{R} = \frac{12V}{2.2\text{ k}\Omega} = 0.0054545\text{ A} = 5.455\text{ mA} \\ \textcircled{5} I &= \frac{V}{R} = \frac{15V}{2.2\text{ k}\Omega} = 0.006818\text{ A} = 6.818\text{ mA} \end{aligned}$$

[3 marks]

- (ii) Change the resistor to $R = 3.3\text{ k}\Omega$, and repeat step (i).

Pre-Lab workspace

$$\begin{aligned} \textcircled{1} I &= \frac{V}{R} = \frac{3V}{3.3\text{ k}\Omega} = 0.000909\text{ A} = 0.909\text{ mA} \\ \textcircled{2} I &= \frac{V}{R} = \frac{6V}{3.3\text{ k}\Omega} = 0.001818\text{ A} = 1.818\text{ mA} \\ \textcircled{3} I &= \frac{V}{R} = \frac{9V}{3.3\text{ k}\Omega} = 0.002727\text{ A} = 2.727\text{ mA} \\ \textcircled{4} I &= \frac{V}{R} = \frac{12V}{3.3\text{ k}\Omega} = 0.003636\text{ A} = 3.636\text{ mA} \\ \textcircled{5} I &= \frac{V}{R} = \frac{15V}{3.3\text{ k}\Omega} = 0.004545\text{ A} = 4.545\text{ mA} \end{aligned}$$

[3 marks]

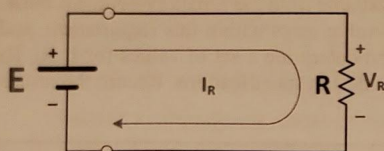


Figure 2.0a: Simple DC Circuit

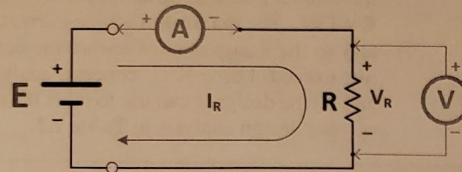


Figure 2.0b: Simple DC Circuit showing Voltmeter & Ammeter connections

R	$V_R \Rightarrow$	3V	6V	9V	12V	15V
		Theory result	Theory result	Theory result	Theory result	Theory Result
2.2 k Ω	$I_R \Rightarrow$ (mA)	1.364mA	2.727mA	4.091mA	5.455mA	6.818mA
3.3 k Ω	$I_R \Rightarrow$ (mA)	0.909mA	1.818mA	2.727mA	3.636mA	4.545mA

Table 2.0: Theoretical results of the Simple DC Circuit in Figure 2.0

[5 marks]

(b) Series Resistors Circuit - KVL

- (i) For the circuit of Figure 2.1a, assume the source-voltage, $E = 15V$, $R_1 = 3.3 k\Omega$, $R_2 = 2.2 k\Omega$ and $R_3 = 1.0 k\Omega$. Determine the expected current, I and the voltages across resistors R_1 ($=V_{ab}$), R_2 ($=V_{bc}$) and R_3 ($=V_{cd}$) for the respective values of resistors shown. Record your theoretical results in Table 2.1. Determine the sum $\Sigma V = (V_{ab} + V_{bc} + V_{cd})$ to verify the KVL law.

Pre-Lab workspace

$R_T = 6.5 k\Omega$ $I_T = 2.308 mA$ $V_T = 15V$
 $R_1 = 3.3 k\Omega$ $I_1 = 2.308 mA$ $V_1 = 7.615V$
 $R_2 = 2.2 k\Omega$ $I_2 = 2.308 mA$ $V_2 = 5.077V$
 $R_3 = 1.0 k\Omega$ $I_3 = 2.308 mA$ $V_3 = 2.308V$

$V_1 = I_1 \times R_1$
 $= 3.3 k\Omega \times 0.0023076$
 $= 7.615V$

$V_2 = I_2 \times R_2$
 $= 2.2 k\Omega \times 0.0023076$
 $= 5.077V$

$V_3 = I_3 \times R_3$
 $= 1.0 k\Omega \times 0.0023076$
 $= 2.308V$

$R_T = R_1 + R_2 + R_3$
 $= 3.3 k\Omega + 2.2 k\Omega + 1.0 k\Omega$
 $= 6.5 k\Omega$

$I = \frac{V}{R} = \frac{15V}{6.5 k\Omega} = 0.0023076 A = 2.308 mA$


[6 marks]

$$V_T = 7.615 + 5.077 + 2.308$$

$$= 15V$$

- (ii) **Design Problem:** Referring to the circuit of **Figure 2.1a**, a designer wishes to create three *equal* potential differences (i.e. $V_{ab} = V_{bc} = V_{cd}$) of **5V** each from a source-voltage, $E = 15V$. The **maximum** source-current, I available from the E battery-source is **5mA**, and so the designer must ensure the current value stays within this requirement, and **not exceed**. Using KVL concept, analyse and determine a set of values for I , R_1 , R_2 and R_3 the designer can use to meet the above design specifications. Record the results of your design analysis in **Table 2.2**.

Pre-Lab workspace

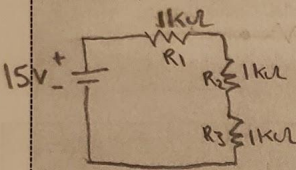

$$I = \frac{V_T}{R_T} = \frac{15V}{3k\Omega} = 5mA$$

$$V_1 = I_1 \times R_1 = 5mA \times 1.0k\Omega = 5V$$

$$V_2 = I_1 \times R_1 = 5mA \times 1.0k\Omega = 5V$$

$$V_3 = I_1 \times R_1 = 5mA \times 1.0k\Omega = 5V$$

$$R_T = R_1 + R_2 + R_3 = 1k\Omega + 1k\Omega + 1k\Omega = 3k\Omega$$

$$V_T = 5V + 5V + 5V = 15V$$

[6 marks]

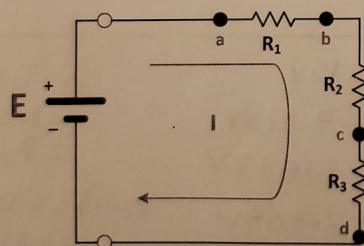


Figure 2.1a: KVL Series Circuit

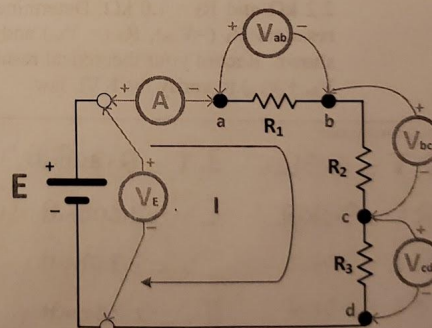


Figure 2.1b: KVL Series Circuit showing Voltmeter & Ammeter connections

V_E	I (mA)	V_{ab} (Volts)	V_{bc} (Volts)	V_{cd} (Volts)	$\Sigma V = (V_{ab} + V_{bc} + V_{cd})$
	Theory result	Theory result	Theory result	Theory result	Theory result
15V	2.308mA	7.615V	5.077V	2.308V	15V

Table 2.1: Theoretical results of the Series Circuit in Figure 2.1a [2.5 marks]

Design values => $R_1 = 1k\Omega$? $R_2 = 1k\Omega$? $R_3 = 1k\Omega$?				
V_E	I (mA)	V_{ab} (Volts)	V_{bc} (Volts)	V_{cd} (Volts)
	Theory result	Theory result	Theory result	Theory result
15V	5mA	5V	5V	5V

Table 2.2: Theoretical results of the *re-designed* Series Circuit in Figure 2.1a [2.5 marks]

(c) Parallel Resistors Circuit - KCL

- (i) For the circuit of Figure 2.2a, assume the source-voltage, $E = 15V$, $R_1 = 3.3 k\Omega$, $R_2 = 2.2 k\Omega$ and $R_3 = 1.0 k\Omega$. Determine the expected currents I , I_1 , I_2 and I_3 as shown in Figure 2.2a. Record your theoretical results in Table 2.3. Determine the sum $\Sigma I = (I_1 + I_2 + I_3)$ to verify the KCL law.

Pre-Lab workspace

$$R_T = 568.966\Omega \quad V_T = 15V \quad I_T = 26.364mA \quad I_T = \frac{V_T}{R_T}$$

$$R_1 = 3.3k\Omega \quad V_1 = 15V \quad I_1 = 4.545mA \quad = \frac{15V}{3.3k\Omega}$$

$$R_2 = 2.2k\Omega \quad V_2 = 15V \quad I_2 = 6.818mA \quad = \frac{15V}{2.2k\Omega}$$

$$R_3 = 1.0k\Omega \quad V_3 = 15V \quad I_3 = 15mA \quad = \frac{15V}{1.0k\Omega}$$

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{3.3k\Omega} + \frac{1}{2.2k\Omega} + \frac{1}{1.0k\Omega}} = 568.966\Omega$$

$$I_1 = \frac{V_1}{R_1} = \frac{15V}{3.3k\Omega} = 4.545mA$$

$$I_2 = \frac{V_2}{R_2} = \frac{15V}{2.2k\Omega} = 6.818mA$$

$$I_3 = \frac{V_3}{R_3} = \frac{15V}{1.0k\Omega} = 15mA$$

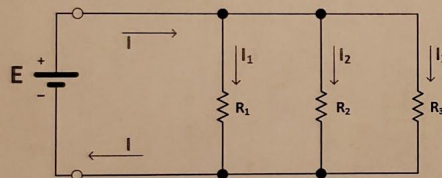


Figure 2.2a: KCL Parallel Circuit

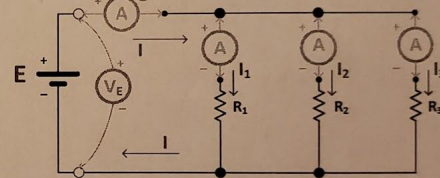


Figure 2.2b: KCL Parallel Circuit with Ammeter & Voltmeter connections

V_E	I (mA)	I_1 (mA)	I_2 (mA)	I_3 (mA)	$\Sigma I = (I_1 + I_2 + I_3)$
	Theory result	Theory result	Theory result	Theory result	Theory result
15V	26.364mA	4.545mA	6.818mA	15mA	26.363mA

Table 2.3: Theoretical results of the Parallel Circuit in Figure 2.2a [6 marks]