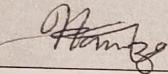


ELE 202  
Electric Circuit Analysis  
LAB COVER PAGE for Part I submission.

Lab #:	3	Lab Title:	Resistive Network Analysis Methods Nodal and mesh
--------	---	------------	--

Last Name:	Malik
First Name:	Hamza

Student #:	S01112545
------------	-----------

Signature:	
------------	---

Section #:	22
Submission date and time:	March 3, 2022 3pm
Due date and time:	March 3, 2022 2pm

Document submission for Part I:

- A completed and signed “COVER PAGE – Part I” has to be included with your submission. The report will not be graded if the signed cover page is not included.
- Your completed handwritten pages of Section 4.0 should be scanned (via a scanner or phone images), together with the required MultiSIM images. **Note:** *MultiSIM results must be generated using the Department’s licensed version of MultiSIM, and the captured screenshots should show your name (at the center-top) and the timestamp (at the bottom-right corner of your screen).*
- Collate and create a **.pdf** or **.docx** file of the above, and upload it via D2L any time prior to the start of your **scheduled lab**. Upload instructions are provided on D2L.

*Zero marks will be assigned for the entire lab if this Part I is not submitted prior to your scheduled lab.*

*\*By signing above, you attest that you have contributed to this submission and confirm that all work you have contributed to this submission is your own work. Any suspicion of copying or plagiarism in this work will result in investigation of Academic Misconduct and may result in a “0” on the work, an “F” in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: [www.ryerson.ca/senate/current/pol60.pdf](http://www.ryerson.ca/senate/current/pol60.pdf).*

## Resistive Network Analysis Methods – Nodal and Mesh


### 1.0 INTRODUCTION

Electric circuit analysis is the process of finding voltages across and currents through every component element in the network. Relatively simple resistive circuits can be analyzed by directly applying Kirchhoff's laws in combination with Ohm's law, as was done in the previous laboratory exercise. However, as the circuits become structurally more complicated and involve increasingly more component elements, this direct method becomes onerous. To aid in the analysis of such complex circuits, two powerful circuit analysis techniques – *nodal* analysis and *mesh* analysis – are commonly used.

*Nodal* analysis is a method of determining the voltage at the nodes in a circuit with respect to a “*reference*” node, using Kirchhoff's Current Law (*KCL*). *Mesh* analysis is a method that is used to solve for the current through any component element in a planar circuit, using Kirchhoff's Voltage Law (*KVL*). Either method used yields the same results; the choice often depends on a personal preference or on the intuitiveness of the analysis method better suited for a particular structural configuration of the circuit elements in a network.

As noted above, *nodal* analysis requires selecting a circuit node as the “*reference*”. The *reference* node is commonly referred to as “*ground*” since it is assumed to have, or be at, *zero* potential. A *reference* node is indicated by any of the three symbols in **Figure 1.0**.

**Figure 1.0:** Common symbols for a *reference* node

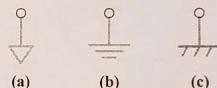

The symbol in **Figure 1.0a** can be used to indicate a “*common ground*” reference node. When the potential of the earth is used as a reference, this common ground symbol can be interchanged with the symbol of an “*earth ground*” in **Figure 1.0b**. For most circuits, the symbol in Figure 1.0b often gets used to denote a common “*ground*” reference node even when not connected to the earth’s potential. The type of ground in **Figure 1.0c** is referred to as a “*chassis ground*” and is used in devices where the case, enclosure, or chassis acts as the reference point for all circuits in the device.

Although *theoretically* the choice of a reference node for a circuit is arbitrary, *practically* the choice for the reference node is often obvious. For example, the node with the most branches is usually a good choice. For more practical circuits, the node that represents the **negative terminal** of an input power source to which most circuit branches connect is often an intuitive “*ground*” reference point to use. All *unreferenced* node voltages in a circuit are then defined in an absolute sense with respect to this “*ground*” reference node.

**References:** (i) Course Textbook: “*Fundamentals of Electric Circuits*” by C. K. Alexander and M. N. O. Sadiku; and (ii) “*Electric Circuits*” by J. W. Nilsson and S. A. Riedel

### 2.0 OBJECTIVES

- To understand the concept of circuit *reference* node.
- To experimentally verify *nodal* and *mesh* analysis techniques on a D.C. resistive circuit.

### 3.0 Required LAB EQUIPMENT & PARTS

- Digital Multimeter (DMM) and Power Supply
- ELE202 Lab Kit: various components, breadboard, wires and jumpers.

## 4.0 PRE-LAB: ASSIGNMENT

### (a) Circuit Reference Node

- (i) For the circuit shown in **Figure 2.0a**, the input D.C. source voltage,  $E = 15 \text{ V}$  and node "d" is selected as the *reference node* connected to the circuit ground,  $V_d = 0 \text{ V}$ . Calculate the current,  $I$  and the voltage at node "a" ( $=V_a$ ), node "b" ( $=V_b$ ), and node "c" ( $=V_c$ ) with respect to the ground *reference node*. From these node voltages, calculate the resistor voltages,  $V_{ab}$ ,  $V_{bc}$ , and  $V_{cd}$  across resistors  $R_1$ ,  $R_2$  and  $R_3$ , respectively. Record all the results in **Table 2.0**.

Pre-Lab workspace




$$\begin{aligned}V_a &= 15 \text{ V} \\V_b &= V^+ - V^- \\&= 15 - 2.308 \\&= 12.692 \text{ V} \\V_c &= V^+ - V^- \\&= 12.692 - 5.077 \\&= 7.615 \text{ V}\end{aligned}$$

Apply KVL

$$\begin{aligned}-15 + I \times (1) + I \times (2.2) + I \times (3.3) &= 0 \\-15 + I \times (3.3 + 2.2 + 1.0) &= 0 \\-15 + I \times (6.5) &= 0 \\I \times (6.5) &= 15 \\I &= 2.308 \text{ mA}\end{aligned}$$
$$\begin{aligned}V_{ab} &= IR = (2.308 \text{ mA})(1 \text{ k}\Omega) = 2.308 \text{ V} \\V_{bc} &= IR = (2.308 \text{ mA})(2.2 \text{ k}\Omega) = 5.077 \text{ V} \\V_{cd} &= IR = (2.308 \text{ mA})(3.3 \text{ k}\Omega) = 7.615 \text{ V}\end{aligned}$$

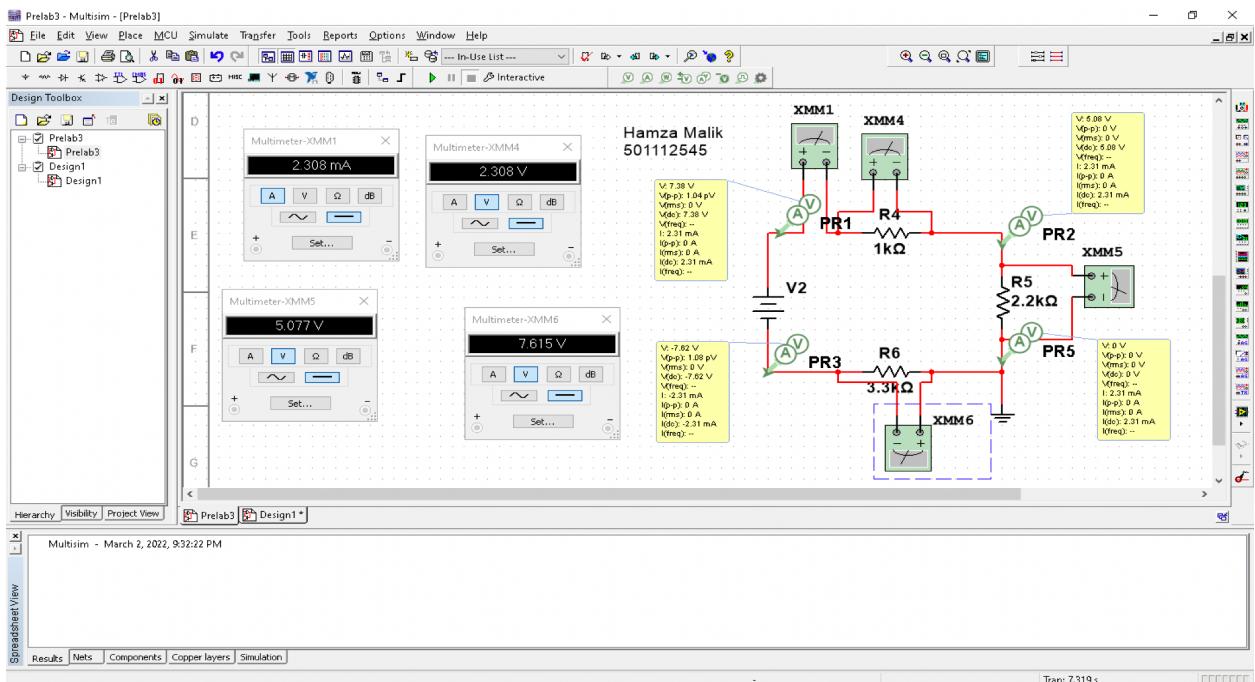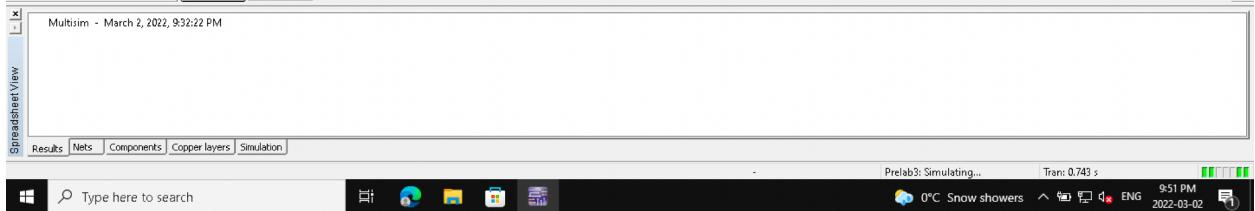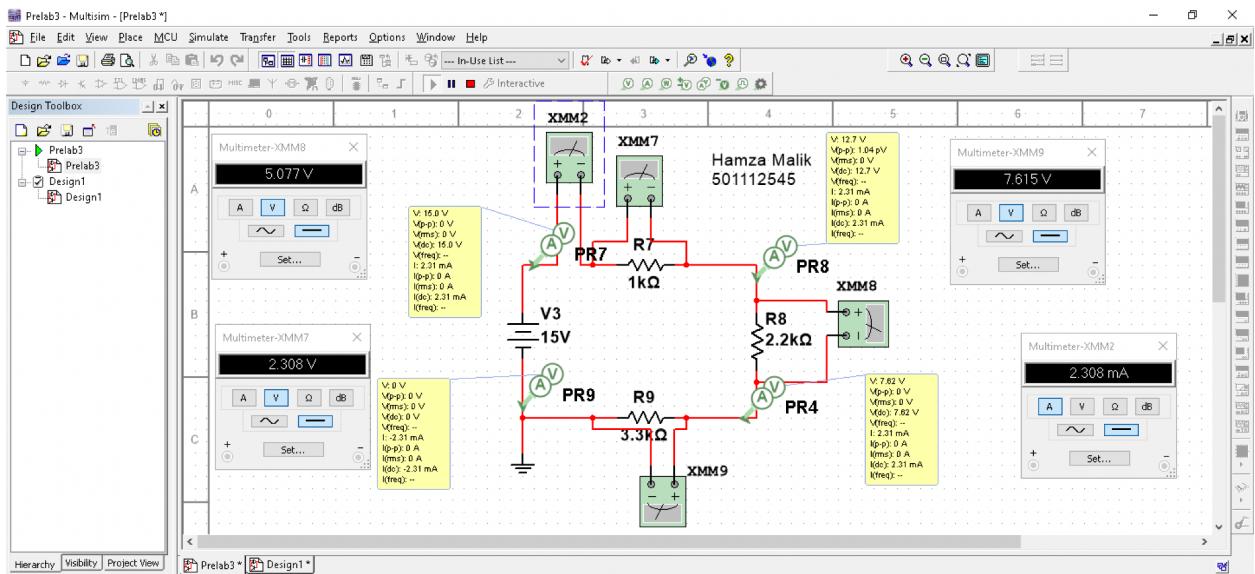- (ii) Construct the circuit of **Figure 2.0a** in MultiSIM. With node "d" as the *reference node*, measure the current,  $I$ , the node voltages  $V_a$ ,  $V_b$  and  $V_c$ , and the voltages across  $R_1$  ( $=V_{ab}$ ),  $R_2$  ( $=V_{bc}$ ), and  $R_3$  ( $=V_{cd}$ ), respectively. Record all the results in **Table 2.0**.

- Copy and paste a screenshot showing one MultiSIM readings on the circuit. Include the MultiSIM circuit file (.ms14) in your Pre-Lab submission.
- All screenshots should show your name printed on the center-top of the MultiSIM screen and the timestamp at the bottom-lower corner.



(iii) **Relocate** the circuit ground *reference node* at node "c" as shown in **Figure 2.0b**, thereby making  $V_c = 0V$ . Then repeat above steps (i) and (ii) but with calculations/measurements of node voltages  $V_a$ ,  $V_b$ , and  $V_d$  with respect to reference node "c"; and circuit element voltages across  $R_1 (=V_{ab})$ ,  $R_2 (=V_{bc})$ , and  $R_3 (=V_{cd})$  as before.

(iv) Comment on the results in **Table 2.0** obtained for both cases (when *reference point* at "d" and *reference point* at "c"). State clearly which one of the currents, node voltages, or element voltages have changed or remain unchanged; and explain why.

Pre-Lab workspace

$$I = 2.308 \text{ mA}, V_c = 0V$$

$$V_{ab} = IR = (2.308 \text{ mA})(1 \text{ k}\Omega) = 2.308 \text{ V}$$

$$V_{bc} = IR = (2.308 \text{ mA})(2.2 \text{ k}\Omega) = 5.077 \text{ V}$$

$$V_{cd} = IR = (2.308 \text{ mA})(3.3 \text{ k}\Omega) = 7.615 \text{ V}$$

$$\begin{aligned} V_a &= V^+ - V^- \\ &= 15 - 7.615 \\ &= 7.385 \text{ V} \end{aligned}$$

$$\begin{aligned} V_b &= V^+ - V^- \\ &= 5.077 - 0 \\ &= 5.077 \text{ V} \end{aligned}$$

$$\begin{aligned} V_d &= V^+ - V^- \\ &= 0 - 7.615 \\ &= -7.615 \text{ V} \end{aligned}$$

For Figure 2.0a and b everything stayed the same except  $V_a$ ,  $V_c$ , and  $V_d$  due to the reference node which caused the voltage across  $V_d$  and  $V_c$  to change.

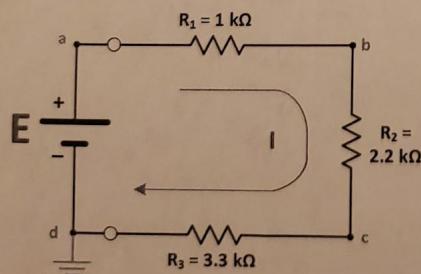


Figure 2.0a: Circuit reference node at "d"

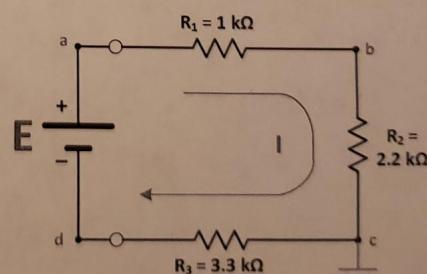


Figure 2.0b: Circuit reference node at "c"

		Using Reference Node "d"	Using Reference Node "c"
$I$ (mA)	Theoretical value => MultiSIM value =>	2.308mA 2.308mA	2.308mA 2.308mA
$V_a$ (Volts)	Theoretical value => MultiSIM value =>	15V 15V	7.385V 7.385V
$V_b$ (Volts)	Theoretical value => MultiSIM value =>	12.692V 12.692V	5.077V 5.077V
$V_c$ (Volts)	Theoretical value => MultiSIM value =>	7.615V 7.615V	0 0
$V_d$ (Volts)	Theoretical value => MultiSIM value =>	0 0	-7.615V -7.615V
$V_{ab}$ (Volts)	Theoretical value => MultiSIM value =>	2.308V 2.308V	2.308V 2.308V
$V_{bc}$ (Volts)	Theoretical value => MultiSIM value =>	5.077V 5.077V	5.077V 5.077V
$V_{cd}$ (Volts)	Theoretical value => MultiSIM value =>	7.615V 7.615V	7.615V 7.615V

Table 2.0: Theoretical and MultiSIM results of the Figure 2.0 circuits

### (b) Nodal and Mesh Analysis

Consider the circuits in Figure 3.0, and assume input power supply,  $E = 15V$ .

- (i) **Nodal Analysis:** Select node "d" as a ground reference node as shown in Figure 3.0a. Using the nodal analysis technique, calculate the node voltages  $V_a$ ,  $V_b$  and  $V_c$ . Using these calculated node voltages, determine the value of the branch current,  $I_x$  and the branch voltage,  $V_x$ . Record all your results in Table 3.0.

Pre-Lab workspace

KCL @ node  $V_a$ :  
 $15V = V_a$

KCL @ node  $V_b$ :  
 $\left(\frac{V_b - V_a}{2.2}\right) + \left(\frac{V_b - V_c}{5.1}\right) + \left(\frac{V_b - 0}{3.3}\right) = 0$   
 $(-\frac{1}{2.2})V_a + (\frac{1}{2.2} + \frac{1}{5.1} + \frac{1}{3.3})V_b + (-\frac{1}{5.1})V_c = 0$   
 $-6.81 + (0.953)V_b - (0.196)V_c = 0$   
 $(0.953)V_b - (0.196)V_c = 6.81 \quad (1)$

KCL @ node  $V_c$   
 $(\frac{V_c - V_a}{1}) + (\frac{V_c - V_b}{5.1}) + (\frac{V_c - 0}{1.0}) = 0$   
 $-V_a + (-\frac{1}{5.1})V_b + (1 + 1 + \frac{1}{1.0})V_c = 0$   
 $-15 - (0.196)V_b + (2.196)V_c = 0$   
 $(0.196)V_b + (2.196)V_c = 15 \quad (2)$

Continued on  
separate  
paper.  
→

b) (i) cont.

$$\textcircled{1} \quad 0.953V_b - 0.196V_c = 6.81$$

$$\textcircled{2} \quad -0.196V_b + 2.196V_c = 15$$

$$\begin{bmatrix} 0.953 & -0.196 \\ -0.196 & 2.196 \end{bmatrix} \begin{bmatrix} V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 6.81 \\ 15 \end{bmatrix}$$

$$\begin{aligned}\Delta &= (0.953)(2.196) - (-0.196)(-0.196) \\ &= (2.0927) - (0.0384) \\ &= 2.0543\end{aligned}$$

$$\begin{aligned}\Delta_1 &= \begin{bmatrix} 6.81 & -0.196 \\ 15 & 2.196 \end{bmatrix} = (6.81)(2.196) - (-0.196)(15) \\ &= (14.95) - (-2.94) \\ &= 17.89\end{aligned}$$

$$\begin{aligned}\Delta_2 &= \begin{bmatrix} 0.953 & 6.81 \\ -0.196 & 15 \end{bmatrix} = (0.953)(15) - (6.81)(-0.196) \\ &= (14.29) - (-1.33) \\ &= 15.62\end{aligned}$$

$$\begin{aligned}V_b &= 17.89 / 2.0543 \\ &= 8.71\end{aligned}$$

$$\begin{aligned}V_c &= 15.62 / 2.0543 \\ &= 7.60\end{aligned}$$

$$\begin{aligned}I_x &= V/R \\ &= 8.71 / 3.3 \\ &= 2.64 A\end{aligned}$$

$$V_x = 7.39 V$$

(ii) **Mesh Analysis:** Using the *mesh analysis* technique on the circuit shown in Figure 3.0b, calculate the mesh currents  $I_A$ ,  $I_B$  and  $I_C$ ; and determine the branch currents,  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_X$ ; and the branch voltage,  $V_X$ . Record all your results in **Table 3.0**.

Pre-Lab workspace	
$\text{mesh 1:}$ $-1S + 2.2(I_A - I_C) + 3.3(I_A - I_B)$ $-1S + I_A(2.2 + 3.3) - I_C(2.2) - I_B(3.3) = 1S \quad \textcircled{1}$ $I_A(S.5) - I_C(2.2) - I_B(3.3) = 1S \quad \textcircled{1}$  $\text{mesh 2:}$ $3.3(I_B - I_A) + S.1(I_B - I_C) + I_B(1.0) = 0$ $I_B(3.3 + S.1 + 1.0) - I_A(3.3) - I_C(S.1) = 0$ $I_B(9.4) - I_A(3.3) - I_C(S.1) = 0 \quad \textcircled{2}$  $\text{mesh 3:}$ $+2.2(I_C - I_A) + 1.0(I_C) + S.1(I_C - I_B) = 0$ $I_C(+2.2 + 1.0 + S.1) + I_A(2.2) - I_B(S.1) = 0$ $I_C(8.3) - I_A(2.2) - I_B(S.1) = 0$  $I_X = I_A - I_B$ $= 2.69$ $V_X = (7.30)(1.0)$ $I_1 = I_A - I_C = 2.86 \text{ mA}$ $I_2 = I_B - I_C$ $= 7.39 \text{ mA}$ $I_3 = I_C = 7.39 \text{ mA}$	$\begin{bmatrix} S.5 & -3.3 & -2.2 \\ -3.3 & 9.4 & -S.1 \\ -2.2 & -S.1 & 8.3 \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} 1S \\ 0 \\ 0 \end{bmatrix}$ $\Delta_1 = \begin{vmatrix} 1S & -3.3 & -2.2 \\ 0 & 9.4 & -S.1 \\ 0 & S.1 & 8.3 \end{vmatrix}$ $\Delta_2 = \begin{vmatrix} S.5 & 1S & -2.2 \\ -3.3 & 0 & -S.1 \\ 2.2 & 0 & 8.3 \end{vmatrix}$ $\Delta_3 = \begin{vmatrix} S.5 & -3.3 & 1S \\ -3.3 & 9.4 & 0 \\ 2.2 & S.1 & 0 \end{vmatrix}$ $I_A = \frac{\Delta_1}{\Delta}$ $= 10.25 \text{ mA}$ $I_C = \frac{\Delta_3}{\Delta}$ $= 7.39 \text{ mA}$ $I_B = \frac{\Delta_2}{\Delta}$ $= 7.61 \text{ mA}$ $I_2 = I_B - I_C$ $= 0.22 \text{ mA}$ $I_3 = I_C = 7.39 \text{ mA}$


(iii) Construct the circuit of Figure 3.0 in MultiSIM. Set the input D.C. source, E to 15V, and node "d" as the ground reference node. Measure the branch currents  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_X$ , the branch voltage,  $V_X$  and the node voltages,  $V_a$ ,  $V_b$  and  $V_c$ . Use the measured branch currents to determine the values of the mesh currents  $I_A$ ,  $I_B$  and  $I_C$ . Record all your results in **Table 3.0**.

- Copy and paste a screenshot showing one MultiSIM readings on the circuit. Include the MultiSIM circuit file (.ms14) in your Pre-Lab submission.
- All screenshots should show your name printed on the center-top of the MultiSIM screen

Compare these MutliSIM simulation results in **Table 3.0** with the calculated theoretical values for the node voltages, mesh currents, branch current  $I_X$ , and branch voltage  $V_X$ . State if the *Nodal* and *Mesh* analysis methods yield the same results for the branch current,  $I_X$  and the branch voltage,  $V_X$ . Why?

Pre-Lab workspace

Everything is different besides the  $I_X$  and  $V_X$  values. This is because in mesh analysis you have to find the current in each mesh which which is not done properly in Multisim.

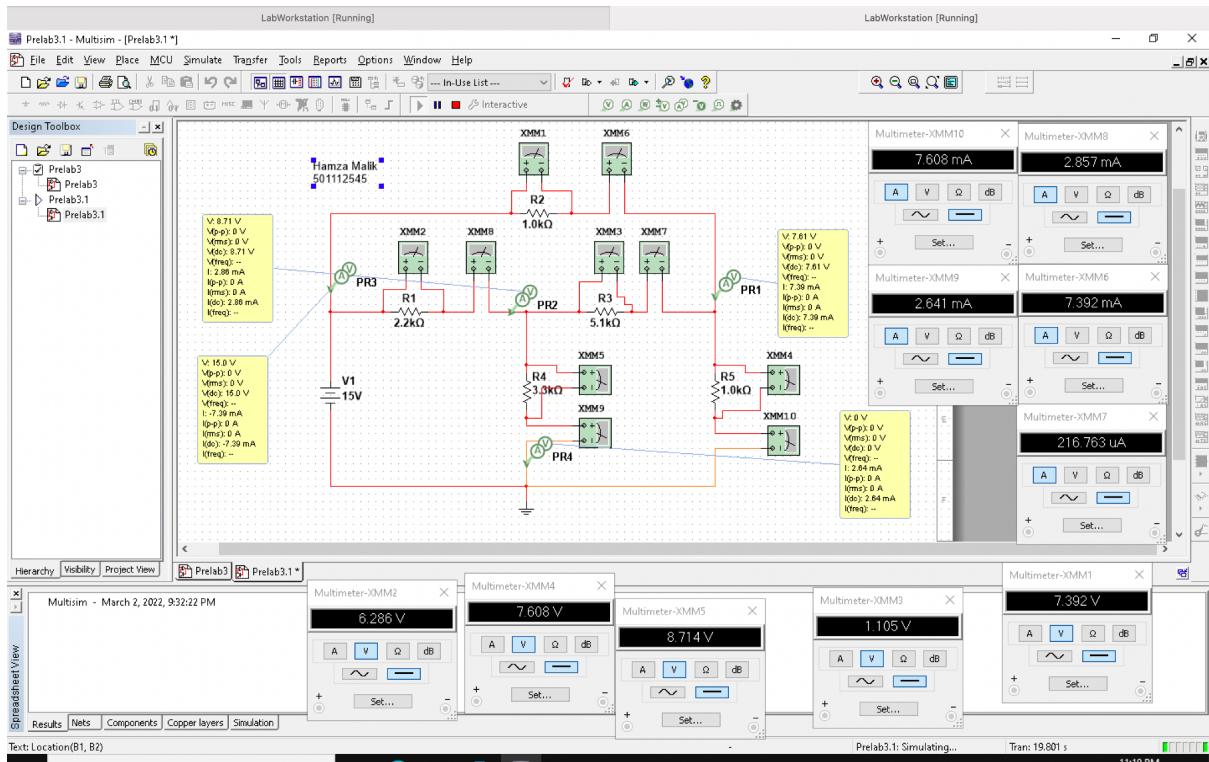

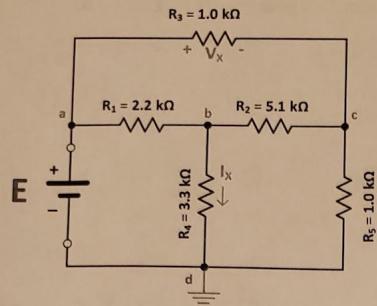


Figure 3.0a: Circuit for Nodal Analysis

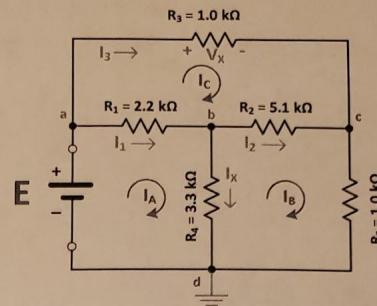


Figure 3.0b: Circuit for Mesh Analysis

		Nodal Analysis	Mesh Analysis
$V_a$ (Volts)	Theoretical value =>	15	
	MultiSIM value =>	15	
$V_b$ (Volts)	Theoretical value =>	8.71	
	MultiSIM value =>	8.71	
$V_c$ (Volts)	Theoretical value =>	7.61	
	MultiSIM value =>	7.61	
$I_A$ (mA)	Theoretical value =>		10.25
	MultiSIM derived =>		10.25
$I_B$ (mA)	Theoretical value =>		7.61
	MultiSIM derived =>		7.61
$I_C$ (mA)	Theoretical value =>		7.39
	MultiSIM derived =>		7.39
$I_X$ (mA)	Theoretical value =>	2.64	2.64
	MultiSIM value =>	2.64	2.64
$V_x$ (Volts)	Theoretical value =>	7.39	7.39
	MultiSIM value =>	7.39	7.39
$I_1$ (mA)	Theoretical value =>		2.86
	MultiSIM value =>		2.86
$I_2$ (mA)	Theoretical value =>		0.22
	MultiSIM value =>		0.22
$I_3$ (mA)	Theoretical value =>		7.39
	MultiSIM value =>		7.39

Table 3.0: Theoretical and MultiSIM results of the Figure 3.0 circuits