

**Ryerson University**

**Department of Electrical, Computer, & Biomedical Engineering**  
Faculty of Engineering & Architectural Science

**ELE 202**  
**Electric Circuit Analysis**

**LAB COVER PAGE for Part I** submission.

<b>Lab #:</b>	2	<b>Lab Title:</b>	Basic Concepts, Relationships and Laws of Electric Circuits
<b>Last Name:</b>	Malik		
<b>First Name:</b>	Hamza		
<b>Student #:</b>	S01112545		
<b>Signature:</b>			

<b>Section #:</b>	10
<b>Submission date and time:</b>	Sunday July 17, 11am
<b>Due date and time:</b>	Monday July 18, 2pm

**Document submission for Part I:**

- A completed and signed “COVER PAGE – **Part I**” has to be included with your submission. The report will not be graded if the signed cover page is not included.
- Your completed handwritten pages of **Section 4.0** should be scanned (via a scanner or phone images), together with the required MultiSIM images. **Note:** *MultiSIM results must be generated using the Department’s licensed version of MultiSIM, and the captured screenshots should show your name (at the center-top) and the timestamp (at the bottom-right corner of your screen).*
- Collate and create a **.pdf** or **.docx** file of the above, and upload it via D2L **any time prior to the start of your scheduled lab**. Upload instructions are provided on D2L.

**Zero marks will be assigned for the entire lab if this Part I is not submitted prior to your scheduled lab.**

\*By signing above, you attest that you have contributed to this submission and confirm that all work you have contributed to this submission is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a “0” on the work, an “F” in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: [www.ryerson.ca/senate/current/pol60.pdf](http://www.ryerson.ca/senate/current/pol60.pdf).



### 3.0 REQUIRED LAB EQUIPMENT & PARTS

- Digital Multimeter (DMM) and Power Supply
- ELE202 Lab Kit:- various components, breadboard, wires and jumpers.

### 4.0 PRE-LAB: ASSIGNMENT

#### (a) *I-V* Characteristics of Ohmic Resistor using a simple D.C. Circuit

- (i) Assume varying values of the DC source-voltage,  $\mathbf{E}$  applied as shown in **Figure 2.0**. For each source-voltage value, use Ohm's Law to determine the corresponding value of the current,  $\mathbf{I}_R$  when the resistance,  $\mathbf{R}$  is  $2.2\text{k}\Omega$  and when it is  $3.3\text{k}\Omega$ . Record your theoretical results in **Table 2.0**.

Pre-Lab workspace


$$\begin{aligned} \textcircled{1} \quad I = \frac{V}{R} = \frac{3V}{2.2k\Omega} = 0.0013636A = 1.363mA \\ \textcircled{2} \quad I = \frac{V}{R} = \frac{6V}{2.2k\Omega} = 0.002727A = 2.727mA \\ \textcircled{3} \quad I = \frac{V}{R} = \frac{9V}{2.2k\Omega} = 0.0040909A = 4.091mA \\ \textcircled{4} \quad I = \frac{V}{R} = \frac{12V}{2.2k\Omega} = 0.0054545A = 5.455mA \\ \textcircled{5} \quad I = \frac{V}{R} = \frac{15V}{2.2k\Omega} = 0.006818A = 6.818mA \end{aligned}$$

- (ii) Construct and simulate this circuit of **Figure 2.0a** on MultiSIM, and set it up as depicted in **Figure 2.0b** to measure the current,  $\mathbf{I}_R$  and voltage,  $\mathbf{V}_R$  when  $\mathbf{R} = 2.2\text{k}\Omega$ . Vary the DC source-voltage,  $\mathbf{E}$  such that the voltage,  $\mathbf{V}_R$  across the resistor has the values listed in **Table 2.0**. For each listed source-voltage, measure the corresponding current,  $\mathbf{I}_R$  and voltage,  $\mathbf{V}_R$ . Record these simulation results in **Table 2.0**.

- Copy and paste a screenshot showing one MultiSIM readings on the circuit. Include the MultiSIM circuit file (.ms14) in your Pre-Lab submission.
- All screenshots should show your name printed on the center-top of the MultiSIM screen and the timestamp at the bottom-lower corner.

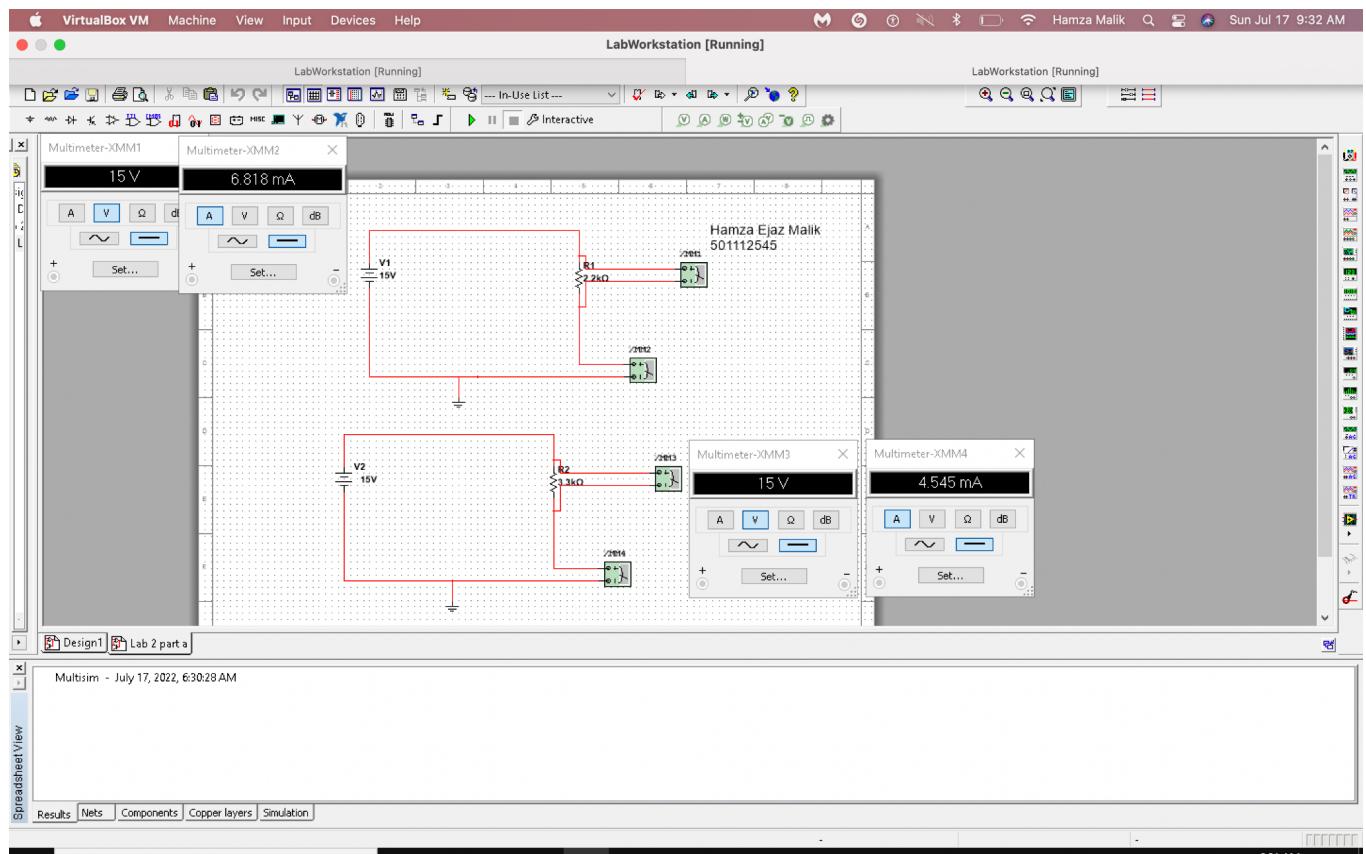- (iii) Change the resistor to  $\mathbf{R} = 3.3\text{k}\Omega$ , and repeat above step (ii).

$$\begin{array}{ll} \textcircled{1} \quad I = \frac{V}{R} = \frac{3V}{3.3k\Omega} = 0.00909A = 0.909mA & \textcircled{4} \quad I = \frac{V}{R} = \frac{12V}{3.3k\Omega} = 0.003636A = 3.636mA \\ \textcircled{2} \quad I = \frac{V}{R} = \frac{6V}{3.3k\Omega} = 0.001818A = 1.818mA & \textcircled{5} \quad I = \frac{V}{R} = \frac{15V}{3.3k\Omega} = 0.004545A = 4.545mA \\ \textcircled{3} \quad I = \frac{V}{R} = \frac{9V}{3.3k\Omega} = 0.002727A = 2.727mA & \end{array}$$





- (iv) Compare your Theory results with the MultiSIM results from **Table 2.0**, and comment on your observations.

Pre-Lab workspace

Comparing both the theory results and the multisim results from table 2.0 we can conclude that the results are exactly the same. Differences that could occur could nearly be due to uncertainty.

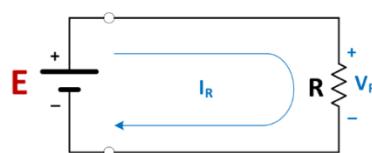


Figure 2.0a: Simple DC Circuit

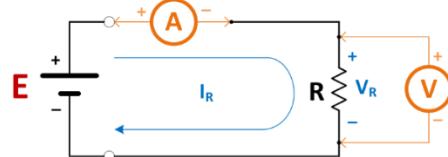


Figure 2.0b: Simple DC Circuit showing Voltmeter & Ammeter connections

<b>R</b>	<b>V<sub>R</sub> =&gt;</b>	<b>3V</b>		<b>6V</b>		<b>9V</b>		<b>12V</b>		<b>15V</b>	
		Theory result	MultiSIM result								
<b>2.2 kΩ</b>	<b>I<sub>R</sub> =&gt; (mA)</b>	1.364mA	1.364mA	2.727mA	2.727mA	4.091mA	4.091mA	5.455mA	5.455mA	6.818mA	6.818mA
<b>3.3 kΩ</b>	<b>I<sub>R</sub> =&gt; (mA)</b>	0.909mA	0.909mA	1.818mA	1.818mA	2.727mA	2.727mA	3.636mA	3.636mA	4.545mA	4.545mA

Table 2.0: Theoretical and MultiSIM results of the Simple DC Circuit in Figure 2.0



### (b) Series Resistors Circuit - KVL

- (i) For the circuit of **Figure 2.1a**, assume the source-voltage,  $\mathbf{E} = 15\text{V}$ ,  $R_1 = 3.3 \text{ k}\Omega$ ,  $R_2 = 2.2 \text{ k}\Omega$  and  $R_3 = 1.0 \text{ k}\Omega$ . Determine the expected current,  $\mathbf{I}$  and the voltages across resistors  $\mathbf{R}_1 (=V_{ab})$ ,  $\mathbf{R}_2 (=V_{bc})$  and  $\mathbf{R}_3 (=V_{cd})$  for the respective values of resistors shown. Record your theoretical results in **Table 2.1**. Determine the sum  $\Sigma V = (V_{ab} + V_{bc} + V_{cd})$  to verify the KVL law.

$\begin{aligned} RT &= 6.5 \text{ k}\Omega \\ R_1 &= 3.3 \text{ k}\Omega \\ R_2 &= 2.2 \text{ k}\Omega \\ R_3 &= 1.0 \text{ k}\Omega \end{aligned}$	$\begin{aligned} I_T &= 2.308 \text{ mA} \\ I_1 &= 2.308 \text{ mA} \\ I_2 &= 2.308 \text{ mA} \\ I_3 &= 2.308 \text{ mA} \end{aligned}$	$\begin{aligned} VT &= 15\text{V} \\ V_1 &= 7.615\text{V} \\ V_2 &= 5.077\text{V} \\ V_3 &= 2.308\text{V} \end{aligned}$	$\begin{aligned} V_1 &= I_1 \times R_1 \\ &= 3.3 \text{ k}\Omega \times 0.002308 \\ &= 7.615\text{V} \\ V_2 &= I_2 \times R_2 \\ &= 2.2 \text{ k}\Omega \times 0.002308 \\ &= 5.077\text{V} \\ V_3 &= I_3 \times R_3 \\ &= 1 \text{ k}\Omega \times 0.002308 \\ &= 2.308\text{V} \end{aligned}$	
		$\begin{aligned} RT &= R_1 + R_2 + R_3 \\ &= 3.3 \text{ k}\Omega + 2.2 \text{ k}\Omega + 1.0 \text{ k}\Omega \\ &= 6.5 \text{ k}\Omega \\ I &= V/R = 15\text{V}/6.5 \text{ k}\Omega = 0.002308 \text{ A} = 2.308 \text{ mA} \end{aligned}$		$\begin{aligned} VT &= 7.615 + 5.077 + 2.308 \\ &= 15\text{V} \end{aligned}$

- (ii) On MultiSIM, construct and simulate the circuit of **Figure 2.1a** using a DC source-voltage,  $\mathbf{E} = 15\text{V}$ ,  $R_1 = 3.3 \text{ k}\Omega$ ,  $R_2 = 2.2 \text{ k}\Omega$  and  $R_3 = 1.0 \text{ k}\Omega$ . The measurement setup for the simulator is depicted in **Figure 2.1b**. Record the measured current,  $\mathbf{I}$  and the voltages across resistors  $\mathbf{R}_1 (=V_{ab})$ ,  $\mathbf{R}_2 (=V_{bc})$  and  $\mathbf{R}_3 (=V_{cd})$  for the respective values of resistors shown. Record your simulation results in **Table 2.1**. Determine the sum  $\Sigma V = (V_{ab} + V_{bc} + V_{cd})$  to verify the KVL law.


- Copy and paste a screenshot showing one MultiSIM reading on the circuit. Include the MultiSIM circuit file (.ms14) in your Pre-Lab submission.
- All screenshots should show your name printed on the center-top of the MultiSIM screen and the timestamp at the bottom-lower corner.

$\begin{aligned} V_{ab} &= 7.615\text{V} \\ V_{bc} &= 5.077\text{V} \\ V_{cd} &= 2.308\text{V} \end{aligned}$	$\begin{aligned} \Sigma V &= 7.615 + 5.077 + 2.308 \\ &= 15\text{V} \end{aligned}$
---------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------

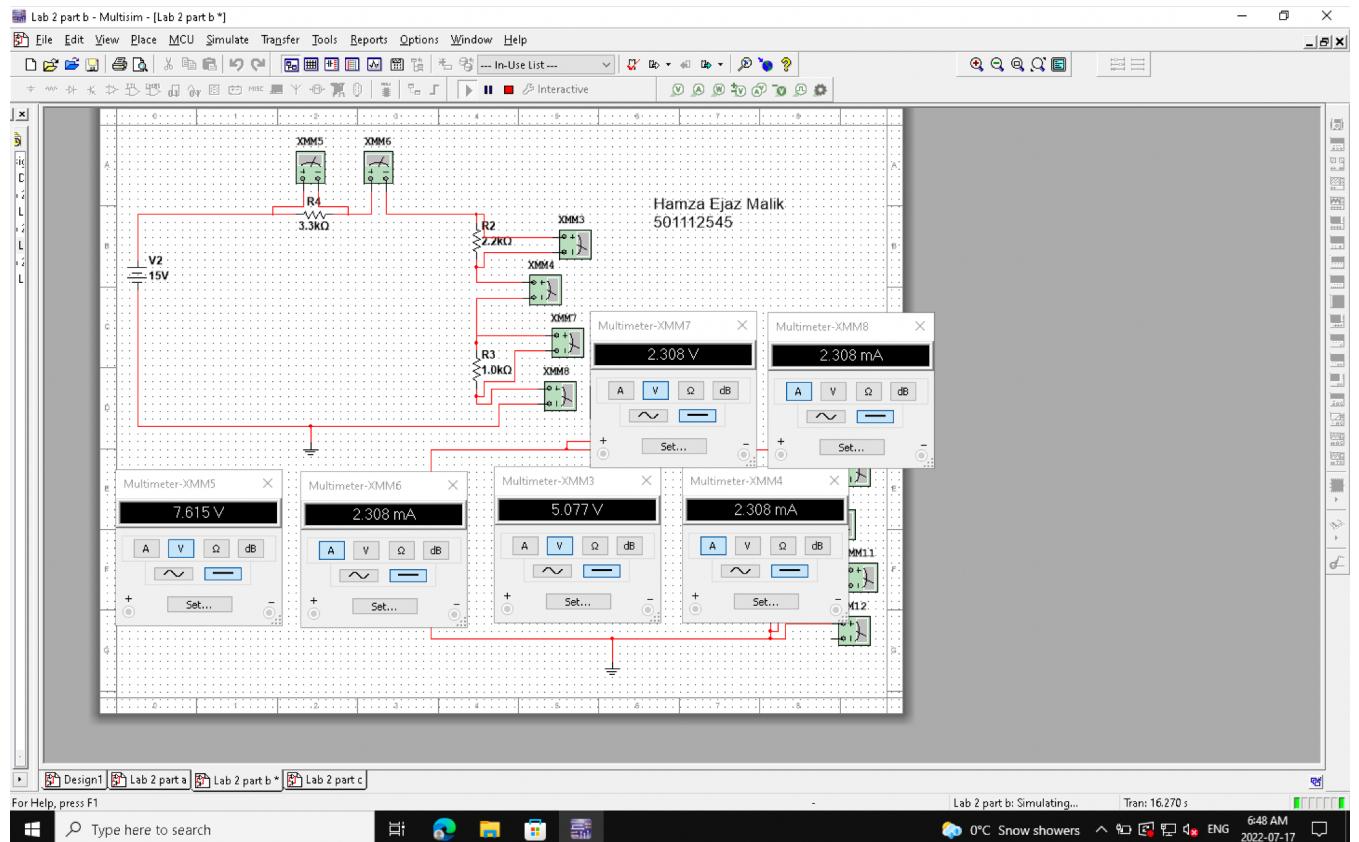- (iii) Compare your Theory results with the MultiSIM results from **Table 2.1**, and comment on your observations.

Pre-Lab workspace

By looking at the theory values and comparing them to the Multisim results, the measured and calculated values are the same. Therefore proves the "KVL" calculations. Any sort of errors could be due to uncertainty in rounding.






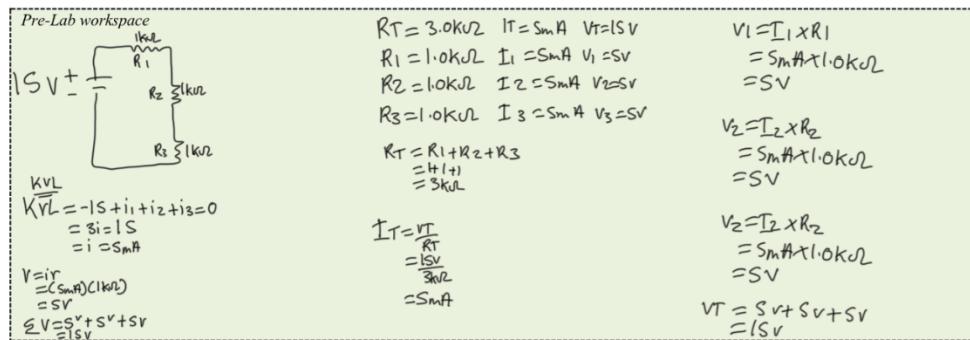(iv) **Design Problem:** Referring to the circuit of **Figure 2.1a**, a designer wishes to create three *equal* potential differences (i.e.  $V_{ab} = V_{bc} = V_{cd}$ ) of **5V** each from a source-voltage, **E = 15V**. The **maximum** source-current, **I** available from the **E** battery-source is **5mA**, and so the designer must ensure the current value stays within this requirement, and **not exceed**. Using KVL concept, analyse and determine a set of values for **I**, **R<sub>1</sub>**, **R<sub>2</sub>** and **R<sub>3</sub>** the designer can use to meet the above design specifications. *Use standard resistor values available in your lab kit in your design.* Record the results of your design analysis in **Table 2.2**.

Using your design values of **R<sub>1</sub>**, **R<sub>2</sub>** and **R<sub>3</sub>** implement and simulate your circuit design on MultiSIM. Measure the current, **I** and the voltages across resistors **R<sub>1</sub>** ( $=V_{ab}$ ), **R<sub>2</sub>** ( $=V_{bc}$ ) and **R<sub>3</sub>** ( $=V_{cd}$ ), and record the results in **Table 2.2**.


- Copy and paste a screenshot showing one MultiSIM readings on the circuit. Include the MultiSIM circuit file (.ms14) in your Pr-Lab submission.
- All screenshots should show your name printed on the center-top of the MultiSIM screen and the timestamp at the bottom-lower corner.





- (v) Compare your Theory results with the MultiSIM results from **Table 2.2**, comment on your observations and explain any discrepancies in your design outcome.

Pre-Lab workspace

Comparing the theory and multisim values I saw that they were exactly the same. This basically indicates that the theory values calculated were correct for the design problem.

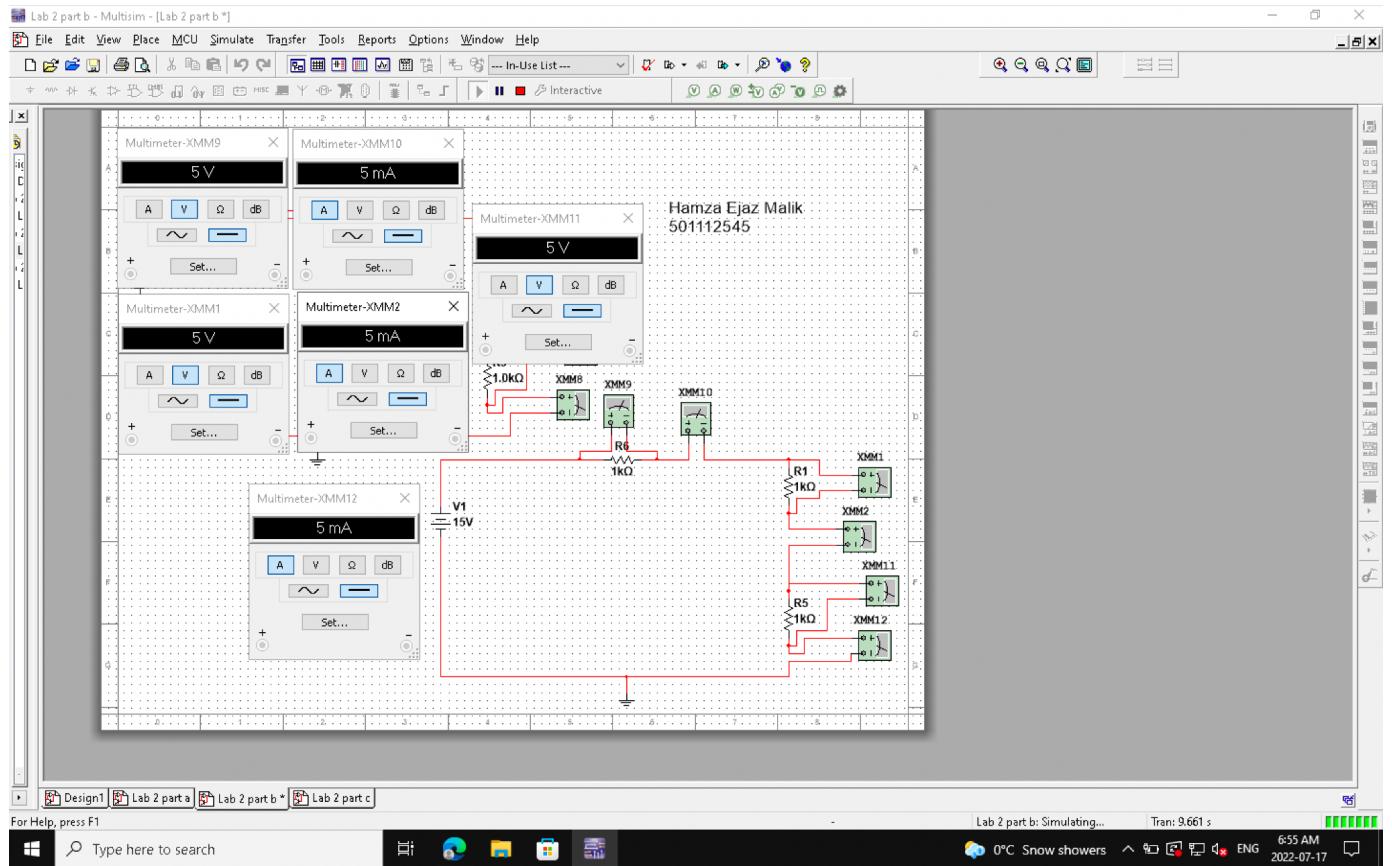

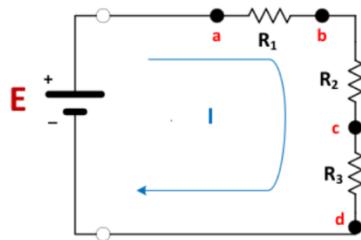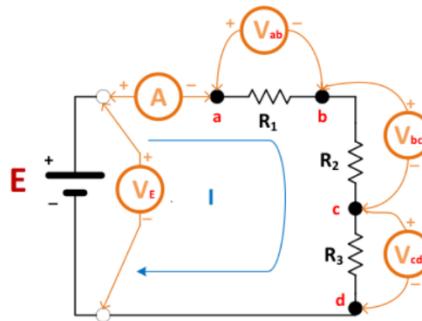**Figure 2.1a:** KVL Series Circuit**Figure 2.1b:** KVL Series Circuit showing Voltmeter & Ammeter connections

<b>V<sub>E</sub></b>	<b>I</b> (mA)		<b>V<sub>ab</sub></b> (Volts)		<b>V<sub>bc</sub></b> (Volts)		<b>V<sub>cd</sub></b> (Volts)		$\Sigma V = (V_{ab} + V_{bc} + V_{cd})$	
	Theory result	MultiSIM result	Theory result	MultiSIM result	Theory result	MultiSIM result	Theory result	MultiSIM result	Theory result	MultiSIM result
<b>15V</b>	2.308mA	2.308mA	7.615V	7.615V	5.077V	5.077V	2.308V	2.308V	15V	15V

**Table 2.1:** Theoretical and MultiSIM results of the Series Circuit in Figure 2.1

Design values => $R_1 = 1k\Omega$ ? $R_2 = 1k\Omega$ ? $R_3 = 1k\Omega$ ?								
<b>V<sub>E</sub></b>	<b>I</b> (mA)		<b>V<sub>ab</sub></b> (Volts)		<b>V<sub>bc</sub></b> (Volts)		<b>V<sub>cd</sub></b> (Volts)	
	Theory result	MultiSIM result	Theory result	MultiSIM result	Theory result	MultiSIM result	Theory result	MultiSIM result
<b>15V</b>	5mA	5mA	5V	5V	5V	5V	5V	5V

**Table 2.2:** Theoretical and MultiSIM results of the *re-designed* Series Circuit in Figure 2.1



### (c) Parallel Resistors Circuit - KCL


- (i) For the circuit of **Figure 2.2a**, assume the source-voltage,  $\mathbf{E} = 15V$ ,  $R_1 = 3.3 \text{ k}\Omega$ ,  $R_2 = 2.2 \text{ k}\Omega$  and  $R_3 = 1.0 \text{ k}\Omega$ . Determine the expected currents  $I_1$ ,  $I_2$  and  $I_3$  as shown in **Figure 2.2a**. Record your theoretical results in **Table 2.3**. Determine the sum  $\Sigma I = (I_1 + I_2 + I_3)$  to verify the KCL law.

Pre-Lab workspace			
KCL @ node a	KCL @ node b	KCL @ node c	
$-15 + 3.3i_1 = 0$	$-15 + 2.2i_2 = 0$	$-15 + 1i_3 = 0$	$V_T = 15V \quad R_T = 568.96\Omega$
$i_1 = \frac{15}{3.3}$	$i_2 = \frac{15}{2.2}$	$i_3 = \frac{15}{1}$	$V_1 = 15V \quad R_1 = 3.3 \text{ k}\Omega$
$I_1 = 4.54 \text{ mA}$	$I_2 = 6.818 \text{ mA}$	$I_3 = 15 \text{ mA}$	$V_2 = 15V \quad R_2 = 2.2 \text{ k}\Omega$
$\sum I = 26.36 \text{ mA}$		$V_3 = 15V \quad R_3 = 1.0 \text{ k}\Omega$	
$R_T = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ $= \frac{1}{3.3 \text{ k}\Omega} + \frac{1}{2.2 \text{ k}\Omega} + \frac{1}{1.0 \text{ k}\Omega}$ $= \frac{1}{0.0017575758} \Omega$ $= 568.96 \Omega$			

- (ii) On MultiSIM, construct and simulate the circuit of **Figure 2.2a** using a DC source-voltage,  $\mathbf{E} = 15V$ ,  $R_1 = 3.3 \text{ k}\Omega$ ,  $R_2 = 2.2 \text{ k}\Omega$  and  $R_3 = 1.0 \text{ k}\Omega$ . The measurement setup for the simulator is depicted in **Figure 2.2b**. Record the measured currents  $I_1$ ,  $I_2$ ,  $I_3$  as shown in **Figure 2.2a**. Record your simulation results in **Table 2.3**. Determine the sum  $\Sigma I = (I_1 + I_2 + I_3)$  to verify the KCL law.

- Copy and paste a screenshot showing one MultiSIM readings on the circuit. Include the MultiSIM circuit file (.ms14) in your Pre-Lab submission.
- All screenshots should show your name printed on the center-top of the MultiSIM screen and the timestamp at the bottom-lower corner.

Pre-Lab workspace	
$I_1 = 4.54 \text{ mA}$	$\sum I = 26.36 \text{ mA}$
$I_2 = 6.818 \text{ mA}$	
$I_3 = 15 \text{ mA}$	

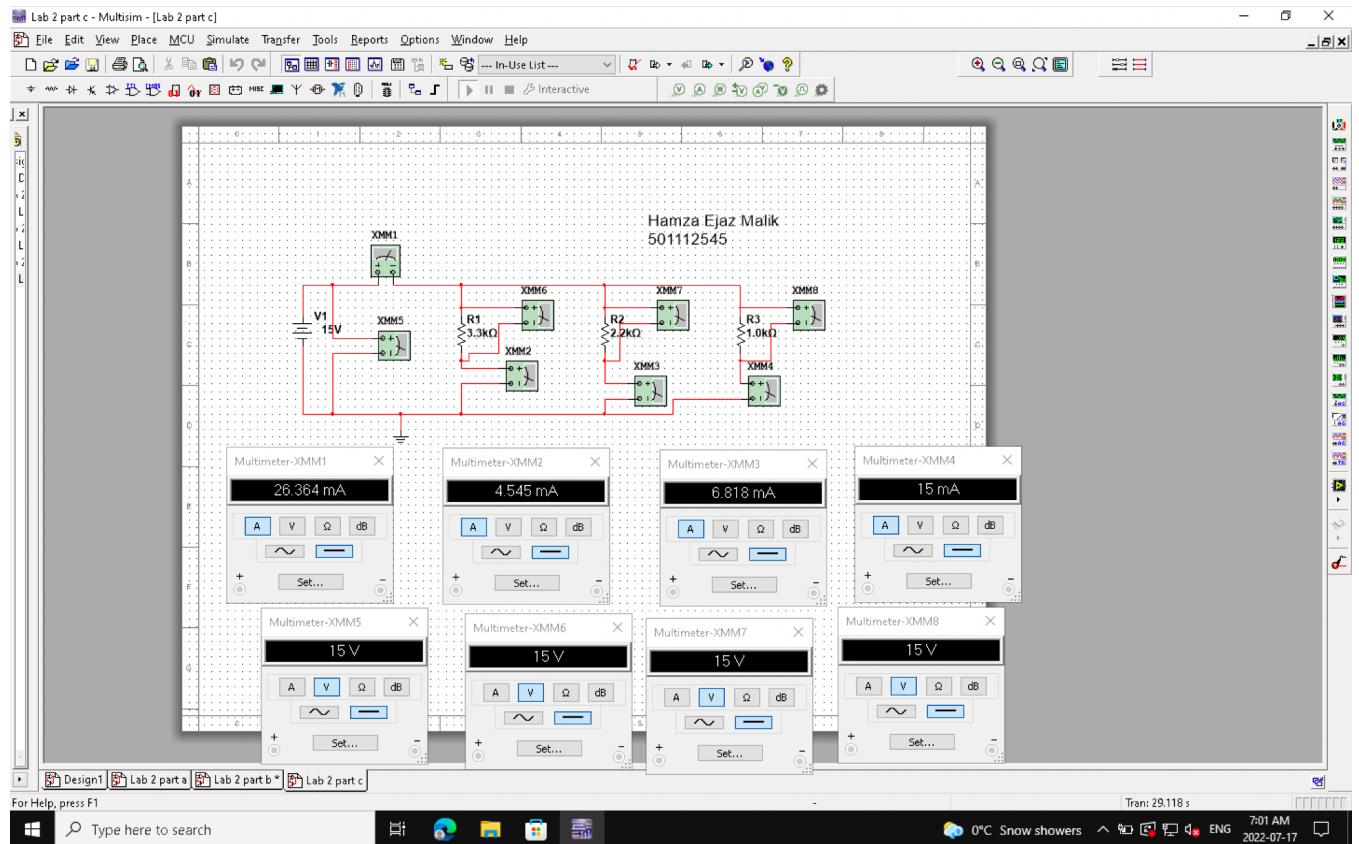



(iii) Compare your Theory results with the MultiSIM results from **Table 2.3**, and comment.

Pre-Lab workspace

While comparing the theoretical and multi-sim values, I saw the values for both are very similar but difference occur due to uncertainty present in the calculated values.

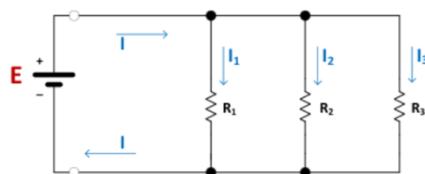


Figure 2.2a: KCL Parallel Circuit

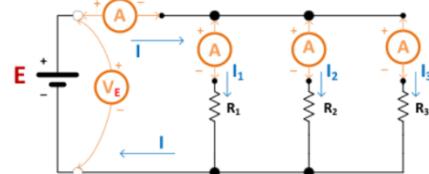


Figure 2.2b: KCL Parallel Circuit with Ammeter & Voltmeter connections

V <sub>E</sub>	I (mA)		I <sub>1</sub> (mA)		I <sub>2</sub> (mA)		I <sub>3</sub> (mA)		$\Sigma I = (I_1 + I_2 + I_3)$	
	Theory result	MultiSIM result	Theory result	MultiSIM result	Theory result	MultiSIM result	Theory result	MultiSIM result	Theory result	MultiSIM result
15V	26.363mA	26.364mA	4.915mA	4.915mA	6.818mA	6.818mA	15mA	15mA	26.363mA	26.364mA

Table 2.3: Theoretical and MultiSIM results of the Parallel Circuit in Figure 2.2